

Taking the indicated derivative, we obtain

$$RI_M e^{j(\omega t + \phi)} + j\omega LI_M e^{j(\omega t + \phi)} = V_M e^{j\omega t}$$

Dividing each term of the equation by the common factor  $e^{j\omega t}$  yields

$$RI_M e^{j\phi} + j\omega LI_M e^{j\phi} = V_M$$

which is an algebraic equation with complex coefficients. This equation can be written as

$$I_M e^{j\phi} = \frac{V_M}{R + j\omega L}$$

Converting the right-hand side of the equation to exponential or polar form produces the equation

$$I_M e^{j\phi} = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} e^{j[-\tan^{-1}(\omega L/R)]}$$

(A quick refresher on complex numbers is given in the Appendix for readers who need to sharpen their skills in this area.) The preceding form clearly indicates that the magnitude and phase of the resulting current are

$$I_M = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}}$$

and

$$\phi = -\tan^{-1} \frac{\omega L}{R}$$

However, since our actual forcing function was  $V_M \cos \omega t$  rather than  $V_M e^{j\omega t}$ , our actual response is the real part of the complex response:

$$\begin{aligned} i(t) &= I_M \cos(\omega t + \phi) \\ &= \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right) \end{aligned}$$

Note that this is identical to the response obtained in the previous example by solving the differential equation for the current  $i(t)$ .

### HINT

Summary of complex number relationships:

$$\begin{aligned} x + jy &= r e^{j\theta} \\ r &= \sqrt{x^2 + y^2} \\ \theta &= \tan^{-1} \frac{y}{x} \\ x &= r \cos \theta \\ y &= r \sin \theta \\ \frac{1}{e^{j\theta}} &= e^{-j\theta} \end{aligned}$$

## 8.3

### Phasors

### HINT

If  $v(t) = V_M \cos(\omega t + \theta)$  and  $i(t) = I_M \cos(\omega t + \phi)$ , then in phasor notation

$$\mathbf{V} = V_M \angle \theta$$

and

$$\mathbf{I} = I_M \angle \phi$$

Once again let us assume that the forcing function for a linear network is of the form

$$v(t) = V_M e^{j\omega t}$$

Then every steady-state voltage or current in the network will have the same form and the same frequency  $\omega$ ; for example, a current  $i(t)$  will be of the form  $i(t) = I_M e^{j(\omega t + \phi)}$ .

As we proceed in our subsequent circuit analyses, we will simply note the frequency and then drop the factor  $e^{j\omega t}$  since it is common to every term in the describing equations. Dropping the term  $e^{j\omega t}$  indicates that every voltage or current can be fully described by a magnitude and phase. For example, a voltage  $v(t)$  can be written in exponential form as

$$v(t) = V_M \cos(\omega t + \theta) = \operatorname{Re}[V_M e^{j(\omega t + \theta)}] \quad 8.18$$

or as a complex number

$$v(t) = \operatorname{Re}(V_M \angle \theta e^{j\omega t}) \quad 8.19$$

Since we are working with a complex forcing function, the real part of which is the desired answer, and each term in the equation will contain  $e^{j\omega t}$ , we can drop  $\operatorname{Re}(\cdot)$  and  $e^{j\omega t}$  and work only with the complex number  $V_M \angle \theta$ . This complex representation is commonly

called a *phasor*. As a distinguishing feature, phasors will be written in boldface type. In a completely identical manner a voltage  $v(t) = V_M \cos(\omega t + \theta) = \text{Re}[V_M e^{j(\omega t + \theta)}]$  and a current  $i(t) = I_M \cos(\omega t + \phi) = \text{Re}[I_M e^{j(\omega t + \phi)}]$  are written in phasor notation as  $\mathbf{V} = V_M/\theta$  and  $\mathbf{I} = I_M/\phi$ , respectively. Note that it is common practice to express phasors with positive magnitudes.

Again, we consider the  $RL$  circuit in Example 8.3. Let us use phasors to determine the expression for the current.

The differential equation is

$$L \frac{di(t)}{dt} + Ri(t) = V_M \cos \omega t$$

The forcing function can be replaced by a complex forcing function that is written as  $\mathbf{V}e^{j\omega t}$  with phasor  $\mathbf{V} = V_M/\theta^\circ$ . Similarly, the forced response component of the current  $i(t)$  can be replaced by a complex function that is written as  $\mathbf{I}e^{j\omega t}$  with phasor  $\mathbf{I} = I_M/\phi$ . From our previous discussions we recall that the solution of the differential equation is the real part of this current.

Using the complex forcing function, we find that the differential equation becomes

$$\begin{aligned} L \frac{d}{dt} (\mathbf{I}e^{j\omega t}) + R\mathbf{I}e^{j\omega t} &= \mathbf{V}e^{j\omega t} \\ j\omega L\mathbf{I}e^{j\omega t} + R\mathbf{I}e^{j\omega t} &= \mathbf{V}e^{j\omega t} \end{aligned}$$

Note that  $e^{j\omega t}$  is a common factor and, as we have already indicated, can be eliminated, leaving the phasors; that is,

$$j\omega L\mathbf{I} + R\mathbf{I} = \mathbf{V}$$

Therefore,

$$\mathbf{I} = \frac{\mathbf{V}}{R + j\omega L} = I_M/\phi = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \angle -\tan^{-1} \frac{\omega L}{R}$$

Thus,

$$i(t) = \frac{V_M}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

which once again is the function we obtained earlier.

## EXAMPLE 8.5

### SOLUTION



The differential equation is reduced to a phasor equation.

We define relations between phasors after the  $e^{j\omega t}$  term has been eliminated as “phasor, or frequency domain, analysis.” Thus, we have transformed a set of differential equations with sinusoidal forcing functions in the time domain into a set of algebraic equations containing complex numbers in the frequency domain. In effect, we are now faced with solving a set of algebraic equations for the unknown phasors. The phasors are then simply transformed back to the time domain to yield the solution of the original set of differential equations. In addition, we note that the solution of sinusoidal steady-state circuits would be relatively simple if we could write the phasor equation directly from the circuit description. In Section 8.4 we will lay the groundwork for doing just that.

Note that in our discussions we have tacitly assumed that sinusoidal functions would be represented as phasors with a phase angle based on a cosine function. Therefore, if sine functions are used, we will simply employ the relationship in Eq. (8.7) to obtain the proper phase angle.

In summary, while  $v(t)$  represents a voltage in the time domain, the phasor  $\mathbf{V}$  represents the voltage in the frequency domain. The phasor contains only magnitude and phase information, and the frequency is implicit in this representation. The transformation from the time domain to the frequency domain, as well as the reverse transformation, is shown in Table 8.1. Recall that the phase angle is based on a cosine function and, therefore, if a sine function is involved, a  $90^\circ$  shift factor must be employed, as shown in the table.