

## 14.1 Laplace Circuit Solutions

To introduce the utility of the Laplace transform in circuit analysis, let us consider the  $RL$  series circuit shown in **Fig. 14.1**. In particular, let us find the current,  $i(t)$ .

Using Kirchhoff's voltage law, we can write the time-domain differential equation,

$$v_s(t) = L \left( \frac{di(t)}{dt} \right) + Ri(t)$$

The complementary differential equation is

$$L \left( \frac{di(t)}{dt} \right) + Ri(t) = 0 \quad 14.1$$

and has the solution

$$i_C(t) = K_C e^{-\alpha t}$$

Substituting  $i_C(t)$  into the complementary equation yields the relationship

$$R - \alpha L = 0$$

or

$$\alpha = \frac{R}{L} = 1000$$

The particular solution is of the same form as the forcing function,  $v_s(t)$ :

$$i_p(t) = K_p$$

Substituting  $i_p(t)$  into the original differential equation yields the expression

$$1 = RK_p$$

or

$$K_p = 1/R = 1/100$$

The final solution is the sum of  $i_p(t)$  and  $i_C(t)$ ,

$$i(t) = K_p + K_C e^{-\alpha t} = \frac{1}{100} + K_C e^{-1000t}$$

To find  $K_C$ , we must use the value of the current at some particular instant of time. For  $t < 0$ , the unit step function is zero and so is the current. At  $t = 0$ , the unit step goes to one; however, the inductor forces the current to instantaneously remain at zero. Therefore, at  $t = 0$ , we can write

$$i(0) = 0 = K_p + K_C$$

or

$$K_C = -K_p = -\frac{1}{100}$$

Thus, the current is

$$i(t) = 10(1 - e^{-1000t})u(t) \text{ mA}$$

Let us now try a different approach to the same problem. Making use of Table 13.2, let us take the Laplace transform of both sides of Eq. (14.1):

$$\mathcal{L}[v_s(t)] = \mathbf{V}_s(s) = L[s\mathbf{I}(s) - i(0)] + R\mathbf{I}(s)$$

**Figure 14.1**

$RL$  series network.

