

## 1.1 System of Units


The system of units we employ is the international system of units, the *Système International des Unités*, which is normally referred to as the SI standard system. This system, which is composed of the basic units meter (m), kilogram (kg), second (s), ampere (A), kelvin (K), and candela (cd), is defined in all modern physics texts and therefore will not be defined here. However, we will discuss the units in some detail as we encounter them in our subsequent analyses.

The standard prefixes that are employed in SI are shown in **Fig. 1.1**. Note the decimal relationship between these prefixes. These standard prefixes are employed throughout our study of electric circuits.

Circuit technology has changed drastically over the years. For example, in the early 1960s the space on a circuit board occupied by the base of a single vacuum tube was about the size of a quarter (25-cent coin). Today that same space could be occupied by an Intel Pentium integrated circuit chip containing 50 million transistors. These chips are the engine for a host of electronic equipment.

**Figure 1.1**

Standard SI prefixes.

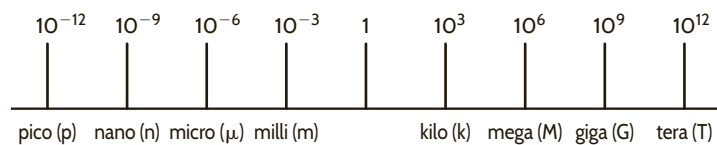

## 1.2 Basic Quantities

Before we begin our analysis of electric circuits, we must define terms that we will employ. However, in this chapter and throughout the book, our definitions and explanations will be as simple as possible to foster an understanding of the use of the material. No attempt will be made to give complete definitions of many of the quantities because such definitions are not only unnecessary at this level but are often confusing. Although most of us have an intuitive concept of what is meant by a circuit, we will simply refer to an *electric circuit* as an interconnection of electrical components, each of which we will describe with a mathematical model.

The most elementary quantity in an analysis of electric circuits is the electric *charge*. Our interest in electric charge is centered around its motion, since charge in motion results in an energy transfer. Of particular interest to us are those situations in which the motion is confined to a definite closed path.

An electric circuit is essentially a pipeline that facilitates the transfer of charge from one point to another. The time rate of change of charge constitutes an electric *current*. Mathematically, the relationship is expressed as

$$i(t) = \frac{dq(t)}{dt} \quad \text{or} \quad q(t) = \int_{-\infty}^t i(x) dx \quad 1.1$$



where  $i$  and  $q$  represent current and charge, respectively (lowercase letters represent time dependency, and capital letters are reserved for constant quantities). The basic unit of current is the ampere (A), and 1 ampere is 1 coulomb per second.

Although we know that current flow in metallic conductors results from electron motion, the conventional current flow, which is universally adopted, represents the movement of positive charges. It is important that the reader think of current flow as the movement of positive charge regardless of the physical phenomena that take place. The symbolism that will be used to represent current flow is shown in **Fig. 1.2**.  $I_1 = 2 \text{ A}$  in **Fig. 1.2a** indicates that at any point in the wire shown, 2 C of charge pass from left to right each second.  $I_2 = -3 \text{ A}$  in **Fig. 1.2b** indicates that at any point in the wire shown, 3 C of charge pass from right to left each second. Therefore, it is important to specify not only the magnitude of the variable representing the current but also its direction.

The two types of current that we encounter often in our daily lives, alternating current (ac) and direct current (dc), are shown as a function of time in **Fig. 1.3**. *Alternating current* is the common current found in every household and is used to run the refrigerator, stove, washing

**Figure 1.2**

Conventional current flow:  
 (a) positive current flow;  
 (b) negative current flow.

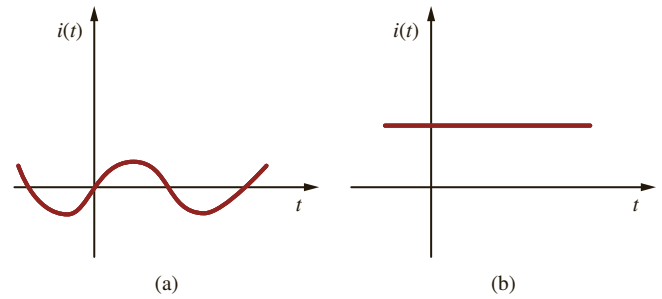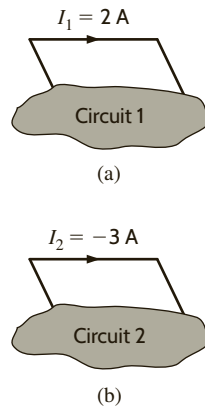
**Figure 1.3**

Two common types of current: (a) alternating current (ac);  
 (b) direct current (dc).

machine, and so on. Batteries, which are used in automobiles and flashlights, are one source of *direct current*. In addition to these two types of currents, which have a wide variety of uses, we can generate many other types of currents. We will examine some of these other types later in the book. In the meantime, it is interesting to note that the magnitude of currents in elements familiar to us ranges from soup to nuts, as shown in **Fig. 1.4**.

We have indicated that charges in motion yield an energy transfer. Now we define the *voltage* (also called the *electromotive force*, or *potential*) between two points in a circuit as the difference in energy level of a unit charge located at each of the two points. Voltage is very similar to a gravitational force. Think about a bowling ball being dropped from a ladder into a tank of water. As soon as the ball is released, the force of gravity pulls it toward the bottom of the tank. The potential energy of the bowling ball decreases as it approaches the bottom. The gravitational force is pushing the bowling ball through the water. Think of the bowling ball as a charge and the voltage as the force pushing the charge through a circuit. Charges in motion represent a current, so the motion of the bowling ball could be thought of as a current. The water in the tank will resist the motion of the bowling ball. The motion of charges in an electric circuit will be impeded or resisted as well. We will introduce the concept of resistance in Chapter 2 to describe this effect.


Work or energy,  $w(t)$  or  $W$ , is measured in joules (J); 1 joule is 1 newton meter ( $\text{N} \cdot \text{m}$ ). Hence, voltage [ $v(t)$  or  $V$ ] is measured in volts (V) and 1 volt is 1 joule per coulomb; that is, 1 volt = 1 joule per coulomb = 1 newton meter per coulomb. If a unit positive charge is moved between two points, the energy required to move it is the difference in energy level between the two points and is the defined voltage. It is extremely important that the variables

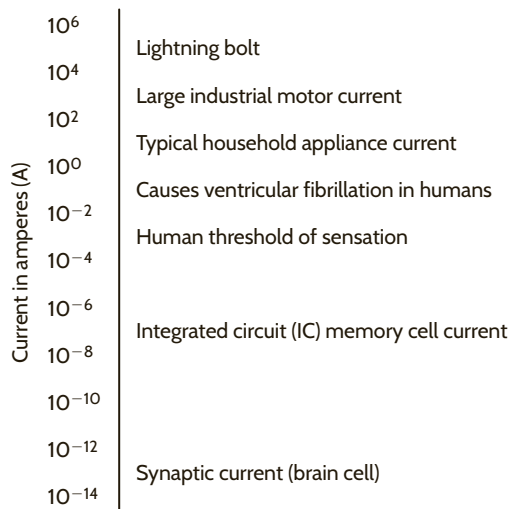**Figure 1.4**

Typical current magnitudes.

**Figure 1.5**

Voltage representations.

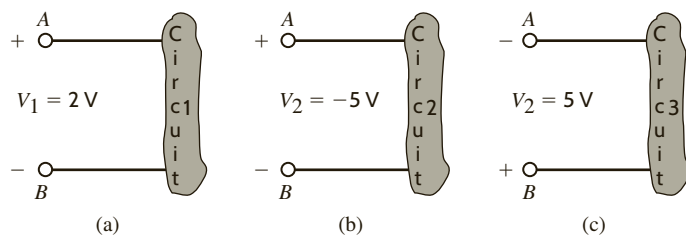

used to represent voltage between two points be defined in such a way that the solution will let us interpret which point is at the higher potential with respect to the other.

In **Fig. 1.5a** the variable that represents the voltage between points *A* and *B* has been defined as  $V_1$ , and it is assumed that point *A* is at a higher potential than point *B*, as indicated by the + and – signs associated with the variable and defined in the figure. The + and – signs define a reference direction for  $V_1$ . If  $V_1 = 2\text{ V}$ , then the difference in potential of points *A* and *B* is 2 V and point *A* is at the higher potential. If a unit positive charge is moved from point *A* through the circuit to point *B*, it will give up energy to the circuit and have 2 J less energy when it reaches point *B*. If a unit positive charge is moved from point *B* to point *A*, extra energy must be added to the charge by the circuit, and hence the charge will end up with 2 J more energy at point *A* than it started with at point *B*.

For the circuit in **Fig. 1.5b**,  $V_2 = -5\text{ V}$  means that the potential between points *A* and *B* is 5 V and point *B* is at the higher potential. The voltage in **Fig. 1.5b** can be expressed as shown in **Fig. 1.5c**. In this equivalent case, the difference in potential between points *A* and *B* is  $V_2 = 5\text{ V}$ , and point *B* is at the higher potential.


Note that it is important to define a variable with a reference direction so that the answer can be interpreted to give the physical condition in the circuit. We will find that it is not possible in many cases to define the variable so that the answer is positive, and we will also find that it is not necessary to do so.

As demonstrated in **Figs. 1.5b** and **c**, a negative number for a given variable, for example,  $V_2$  in **Fig. 1.5b**, gives exactly the same information as a positive number; that is,  $V_2$  in **Fig. 1.5c**, except that it has an opposite reference direction. Hence, when we define either current or voltage, it is absolutely necessary that we specify both magnitude and direction. Therefore, it is incomplete to say that the voltage between two points is 10 V or the current in a line is 2 A, since only the magnitude and not the direction for the variables has been defined.


The range of magnitudes for voltage, equivalent to that for currents in **Fig. 1.4**, is shown in **Fig. 1.6**. Once again, note that this range spans many orders of magnitude.

At this point we have presented the conventions that we employ in our discussions of current and voltage. *Energy* is yet another important term of basic significance. Let's investigate the voltage–current relationships for energy transfer using the flashlight shown in **Fig. 1.7**. The basic elements of a flashlight are a battery, a switch, a light bulb, and connecting wires. Assuming a good battery, we all know that the light bulb will glow when the switch is closed. A current now flows in this closed circuit as charges flow out of the positive terminal of the battery through the switch and light bulb and back into the negative terminal of the battery. The current heats up the filament in the bulb, causing it to glow and emit light. The light bulb converts electrical energy to thermal energy; as a result, charges passing through the bulb lose energy. These charges acquire energy as they pass through the battery as chemical energy is converted to electrical energy. An energy conversion process is occurring in the flashlight as the chemical energy in the battery is converted to electrical energy, which is then converted to thermal energy in the light bulb.


Let's redraw the flashlight as shown in **Fig. 1.8**. There is a current  $I$  flowing in this diagram. Since we know that the light bulb uses energy, the charges coming out of the bulb have less energy than those entering the light bulb. In other words, the charges expend energy as they move through the bulb. This is indicated by the voltage shown across the bulb. The charges gain energy as they pass through the battery, which is indicated by the voltage across the battery. Note the voltage–current relationships for the battery and bulb. We know that the bulb is absorbing energy; the current is entering the positive terminal of the voltage. For

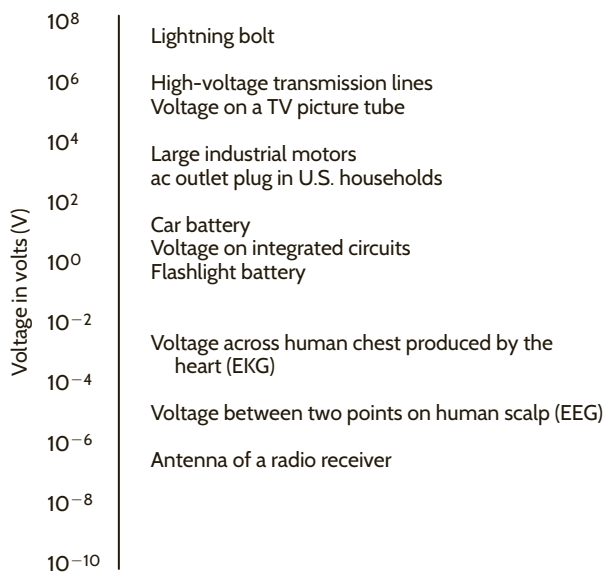**Figure 1.6**


Typical voltage magnitudes.

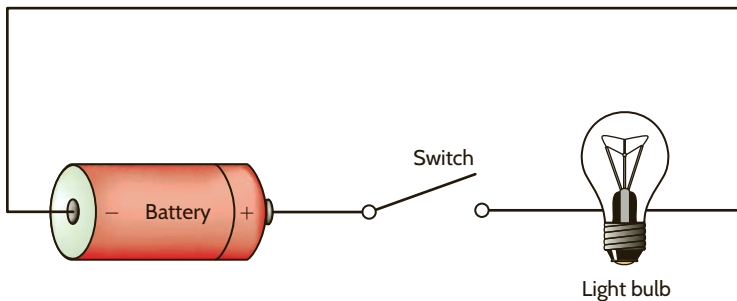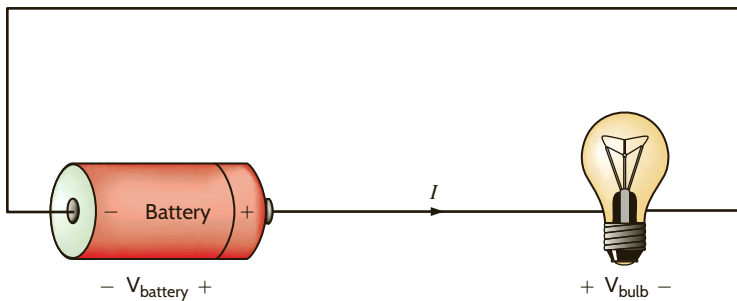**Figure 1.7**


Flashlight circuit.

**Figure 1.8**

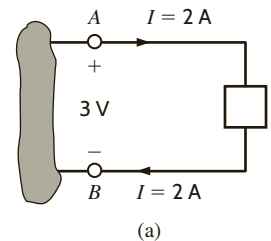Flashlight circuit with voltages and current.



(a)

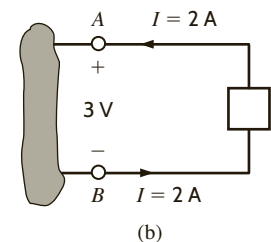

(b)

**Figure 1.9**

Voltage-current relationships for (a) energy absorbed and (b) energy supplied.

the battery, the current is leaving the positive terminal, which indicates that energy is being supplied.

This is further illustrated in **Fig. 1.9**, where a circuit element has been extracted from a larger circuit for examination. In **Fig. 1.9a**, energy is being supplied *to* the element by whatever is attached to the terminals. Note that 2 A—that is, 2 C of charge—are moving from point A to point B through the element each second. Each coulomb loses 3 J of energy as it passes through the element from point A to point B. Therefore, the element is absorbing 6 J of energy per second. Note that when the element is *absorbing* energy, a positive current enters the positive terminal. In **Fig. 1.9b** energy is being supplied *by* the element to whatever is connected to terminals A-B. In this case, note that when the element is *supplying* energy, a positive current enters the negative terminal and leaves via the positive terminal. In this convention, a negative current in one direction is equivalent to a positive current in the opposite direction, and vice versa. Similarly, a negative voltage in one direction is equivalent to a positive voltage in the opposite direction.


**EXAMPLE 1.1****SOLUTION**

Suppose that your car will not start. To determine whether the battery is faulty, you turn on the light switch and find that the lights are very dim, indicating a weak battery. You borrow a friend's car and a set of jumper cables. However, how do you connect his car's battery to yours? What do you want his battery to do?


Essentially, his car's battery must supply energy to yours, and therefore it should be connected in the manner shown in **Fig. 1.10**. Note that the positive current leaves the positive terminal of the good battery (supplying energy) and enters the positive terminal of the weak battery (absorbing energy). Note that the same connections are used when charging a battery.

**Figure 1.10**

Diagram for Example 1.1.

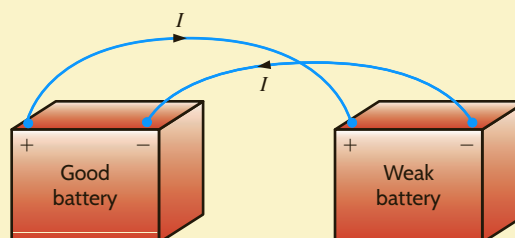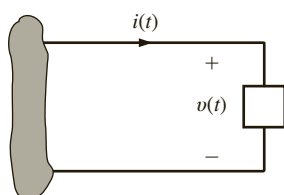

In practical applications, there are often considerations other than simply the electrical relations (e.g., safety). Such is the case with jump-starting an automobile. Automobile batteries produce explosive gases that can be ignited accidentally, causing severe physical injury. Be safe—follow the procedure described in your auto owner's manual.

**Figure 1.11**

Sign convention for power.

We have defined voltage in joules per coulomb as the energy required to move a positive charge of 1 C through an element. If we assume that we are dealing with a differential amount of charge and energy, then

$$v = \frac{dw}{dq} \quad 1.2$$

Multiplying this quantity by the current in the element yields

$$vi = \frac{dw}{dq} \left( \frac{dq}{dt} \right) = \frac{dw}{dt} = p \quad 1.3$$

which is the time rate of change of energy or power measured in joules per second, or watts (W). Since, in general, both  $v$  and  $i$  are functions of time,  $p$  is also a time-varying quantity. Therefore, the change in energy from time  $t_1$  to time  $t_2$  can be found by integrating Eq. (1.3); that is,


$$\Delta w = \int_{t_1}^{t_2} p \, dt = \int_{t_1}^{t_2} vi \, dt \quad 1.4$$

At this point, let us summarize our sign convention for power. To determine the sign of any of the quantities involved, the variables for the current and voltage should be arranged as shown in **Fig. 1.11**. The variable for the voltage  $v(t)$  is defined as the voltage across the element with the positive reference at the same terminal that the current variable  $i(t)$  is entering. This convention is called the *passive sign convention* and will be so noted in the remainder of this book. The product of  $v$  and  $i$ , with their attendant signs, will determine the magnitude and sign of the power. If the sign of the power is positive, power is being absorbed by the element; if the sign is negative, power is being supplied by the element.

**HINT**

The passive sign convention is used to determine whether power is being absorbed or supplied.

Given the two diagrams shown in **Fig. 1.12**, determine whether the element is absorbing or supplying power and how much.

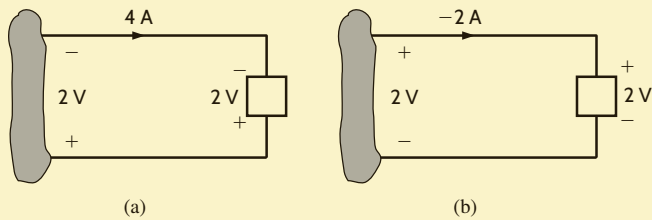

**Figure 1.12**


Elements for  
Example 1.2.

In **Fig. 1.12a**, the power is  $P = (2\text{ V})(-4\text{ A}) = -8\text{ W}$ . Therefore, the element is supplying power. In **Fig. 1.12b**, the power is  $P = (2\text{ V})(-2\text{ A}) = -4\text{ W}$ . Therefore, the element is supplying power.

**SOLUTION**

## LEARNING ASSESSMENT

**E1.1** Determine the amount of power absorbed or supplied by the elements in Fig. E1.1.

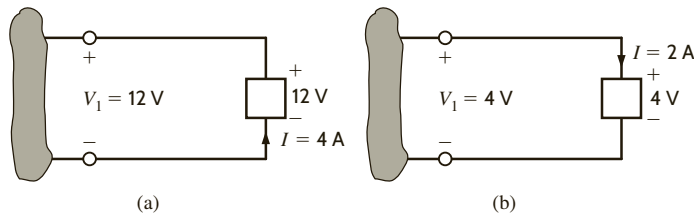


**Figure E1.1**

**ANSWER:**

- (a)  $P = -48\text{ W}$ ;  
(b)  $P = 8\text{ W}$ .

We wish to determine the unknown voltage or current in **Fig. 1.13**.

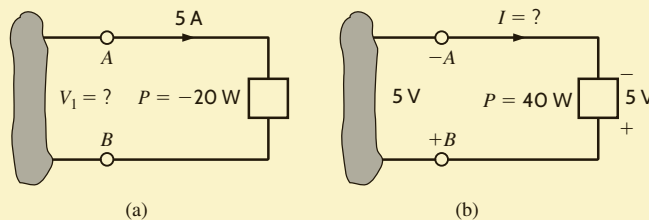

**Figure 1.13**

Elements for  
Example 1.3.


In **Fig. 1.13a**, a power of  $-20\text{ W}$  indicates that the element is delivering power. Therefore, the current enters the negative terminal (terminal A), and from Eq. (1.3) the voltage is  $4\text{ V}$ . Thus, B is the positive terminal, A is the negative terminal, and the voltage between them is  $4\text{ V}$ .

In **Fig. 1.13b**, a power of  $+40\text{ W}$  indicates that the element is absorbing power and, therefore, the current should enter the positive terminal B. The current thus has a value of  $-8\text{ A}$ , as shown in the figure.

**SOLUTION**

## LEARNING ASSESSMENT

**E1.2** Determine the unknown variables in Fig. E1.2.

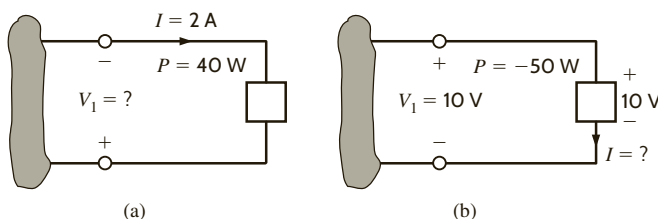

**Figure E1.2**

**ANSWER:**

- (a)  $V_1 = -20\text{ V}$ ;  
(b)  $I = -5\text{ A}$ .